

CIRCUITS

$$\text{Voltage (V)} = \text{units volts (V)} = \frac{\text{J}}{\text{C}}$$

$$\text{Current (I)} = \text{units amps (A)} = \frac{\text{C}}{\text{s}}$$

$$\text{Resistance (R)} = \text{units ohms } (\Omega) = \frac{\text{J} \cdot \text{s}}{\text{C}^2}$$


$$\text{Ohm's Law: } V = I \cdot R$$


$$I = \frac{V}{R}$$

Resistance in series: $R_{TOT} = R_1 + R_2 + R_3 \dots$

Resistance in parallel: $\frac{1}{R_{TOT}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots$

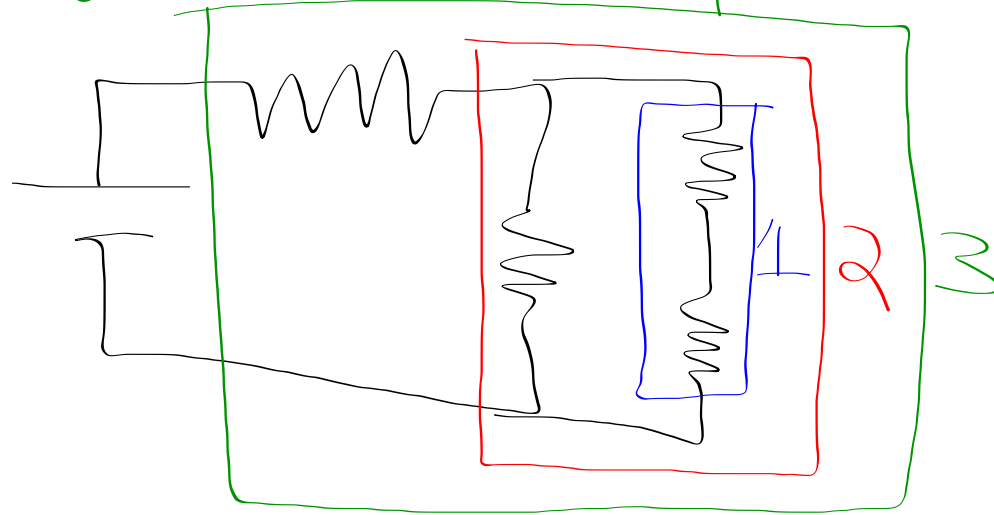Mix: Find "equivalent resistance" of different path



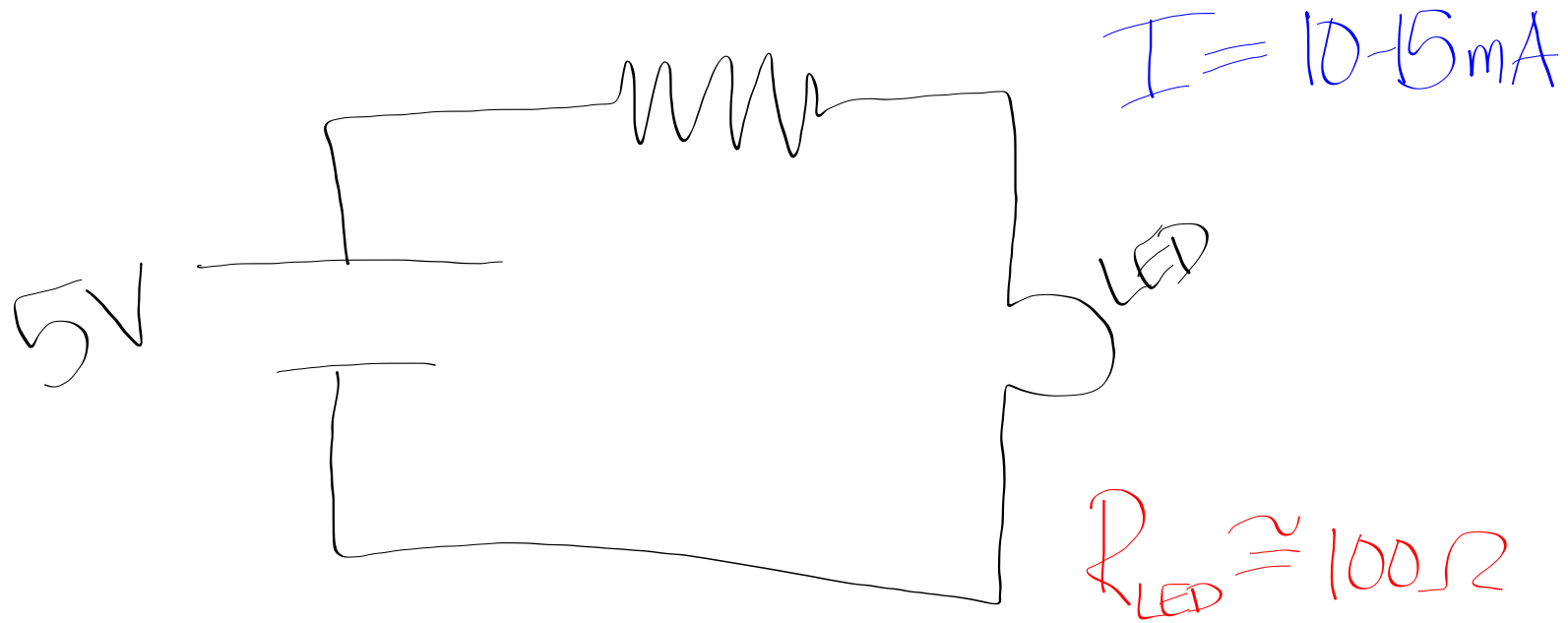

5V Power supply

LED #1 : 10 mA

LED #2 : 15 mA

Build this