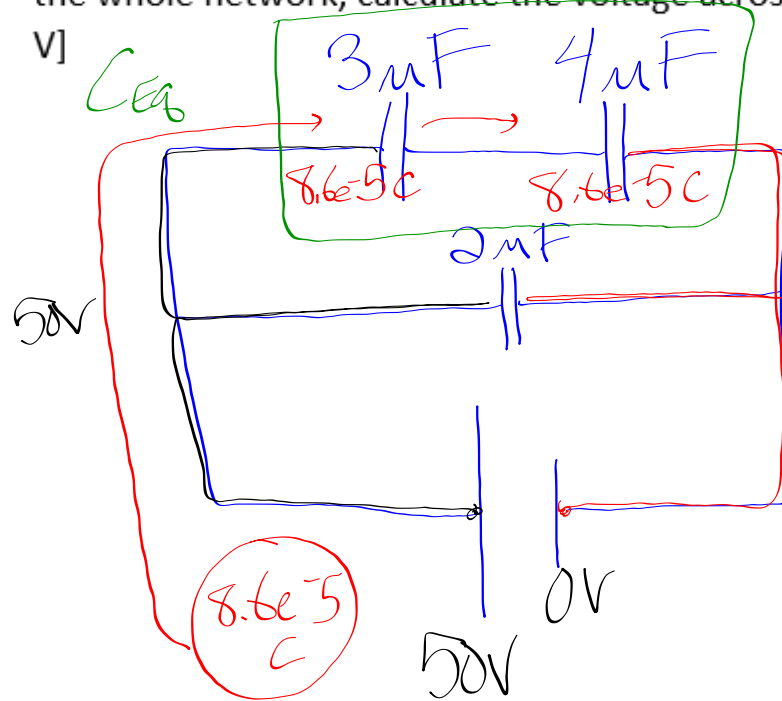


3. A $3.0 \mu\text{F}$ and a $4.0 \mu\text{F}$ capacitor are connected in series to a 9.0V battery and this combination is connected in parallel to a $2.0 \mu\text{F}$ capacitor. (a) What is the net capacitance? (b) if 50V is applied across the whole network, calculate the voltage across each capacitor. [(a) $3.71 \mu\text{F}$; (b) $V_3 = 28.6 \text{ V}$, $V_4 = 21.4 \text{ V}$]



$$C_T = 2\mu\text{F} + \frac{1}{\frac{1}{3\mu\text{F}} + \frac{1}{4\mu\text{F}}}$$


$$3.71\mu\text{F} = 2\mu\text{F} + \boxed{1.71\mu\text{F}}$$

\parallel
 C_{eq}


$$Q = CV$$

$$8.6e-5 \text{ C} = (3e-6 \text{ F}) V = 8.6e-5 \text{ C}$$


$$\boxed{V_3 = 28.7}$$

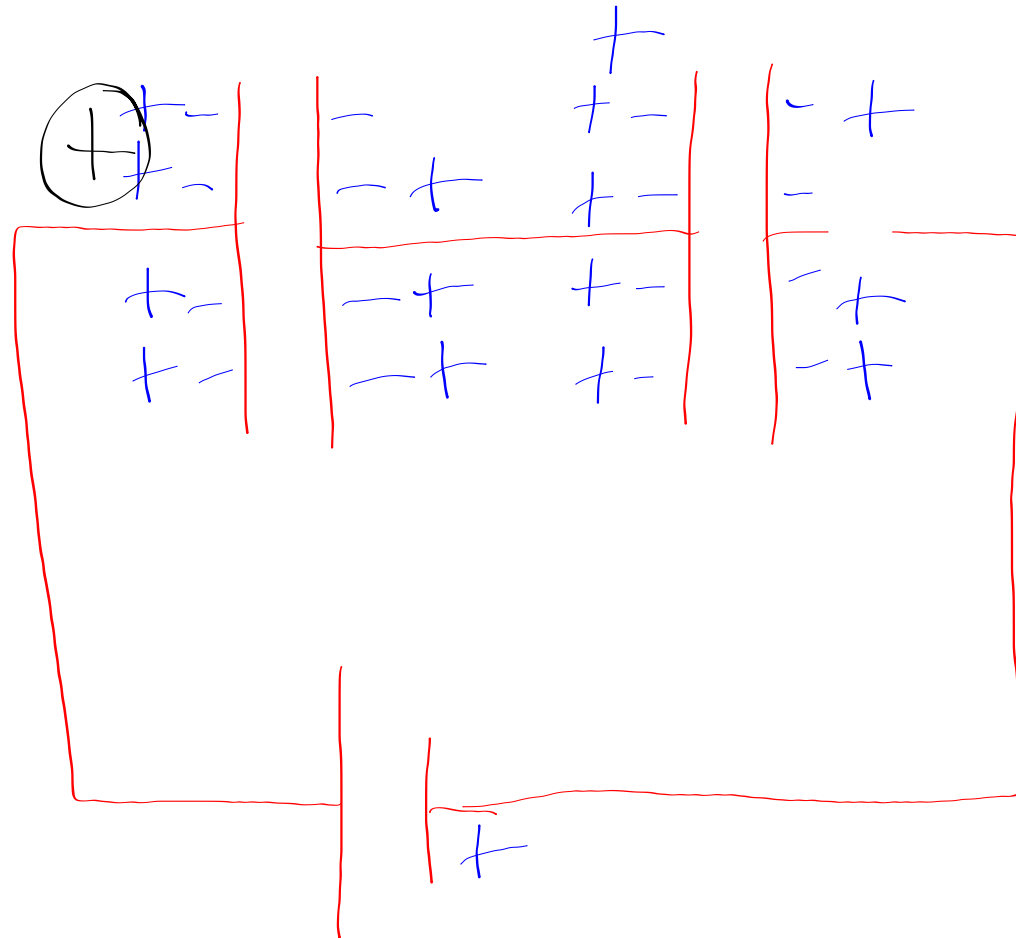

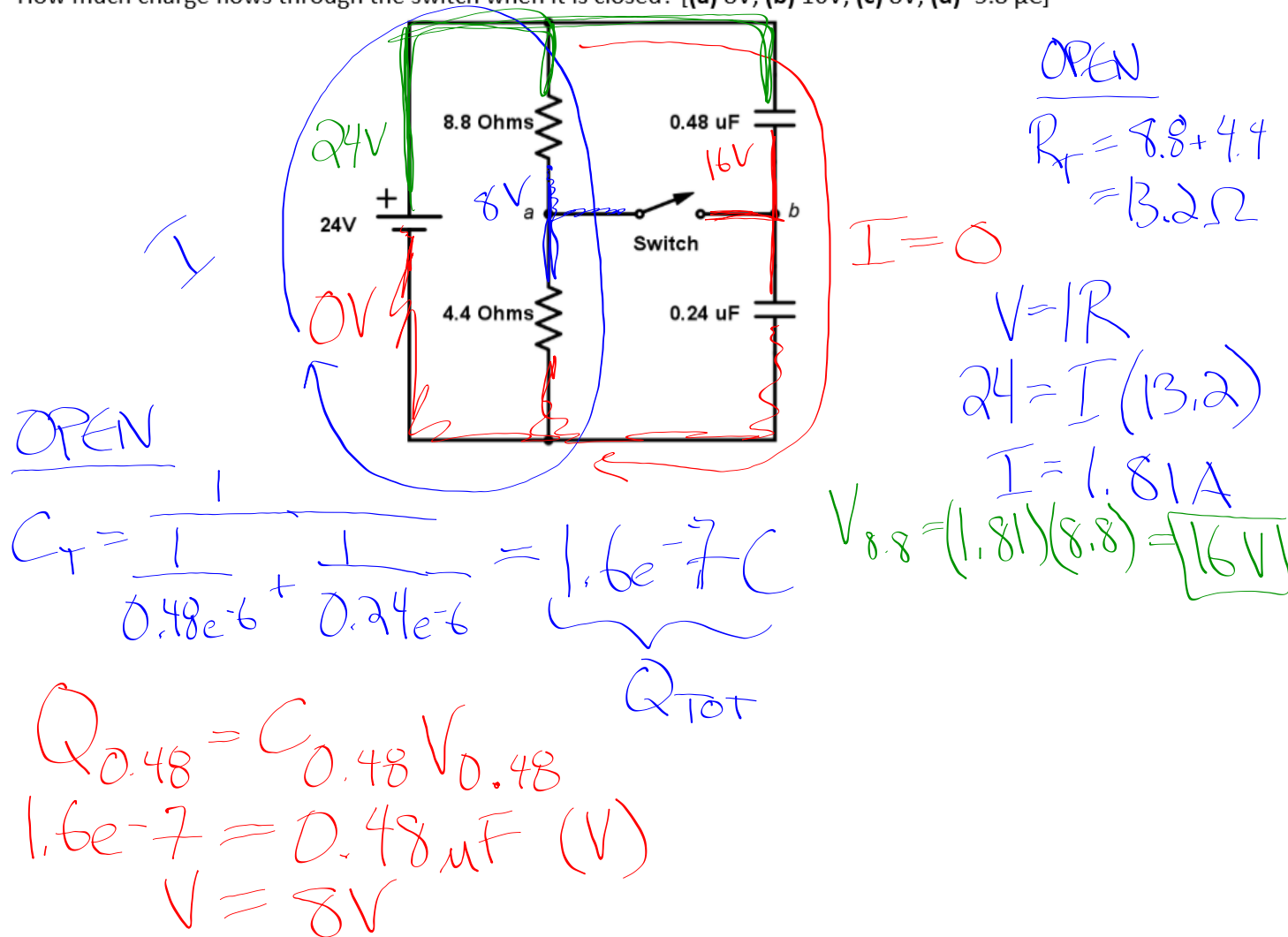4. Two resistors and two capacitors are arranged as in the circuit below. At its steady state (after the capacitors are fully charged), with a potential difference of 24V from the power source, (a) what is the potential at point *a* with the switch open? (b) What is the potential at point *b* with the switch open? (c) When the switch is closed, at the steady state of the circuit, what is the final potential of point *b*? (d) How much charge flows through the switch when it is closed? [(a) 8V; (b) 16V; (c) 8V; (d) -5.8 μC]




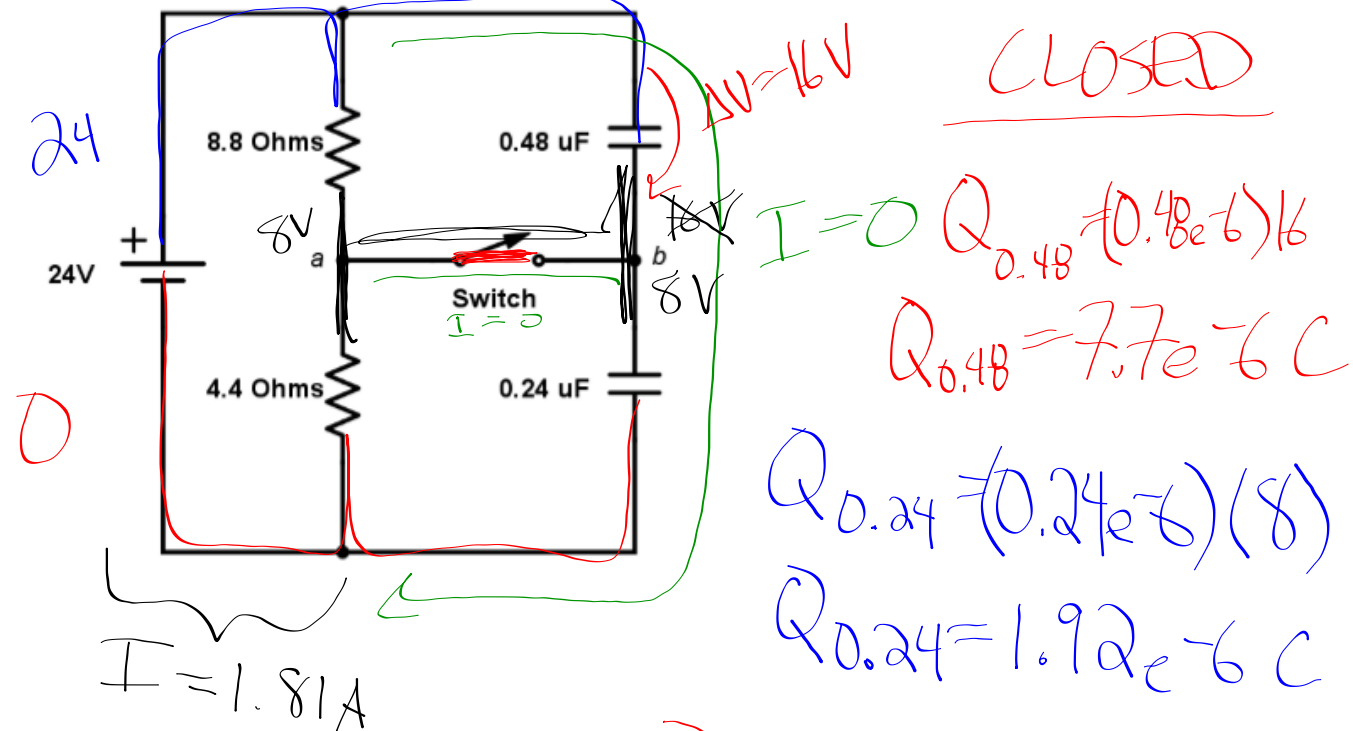
4. Two resistors and two capacitors are arranged as in the circuit below. At its steady state (after the capacitors are fully charged), with a potential difference of 24V from the power source, (a) what is the potential at point *a* with the switch open? (b) What is the potential at point *b* with the switch open? (c) When the switch is closed, at the steady state of the circuit, what is the final potential of point *b*? (d) How much charge flows through the switch when it is closed? [(a) 8V; (b) 16V; (c) 8V; (d) $-5.8 \mu\text{C}$]



$$\left. \begin{array}{l} \Delta Q_{0.48} = 7.54e-6 \text{ C} \\ \Delta Q_{0.24} = 1.76e-6 \text{ C} \end{array} \right\} 5.8e-6 \text{ C}$$

RC Circuits

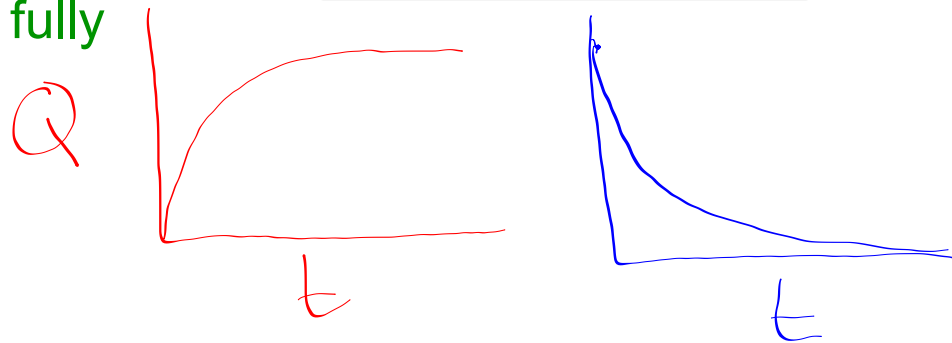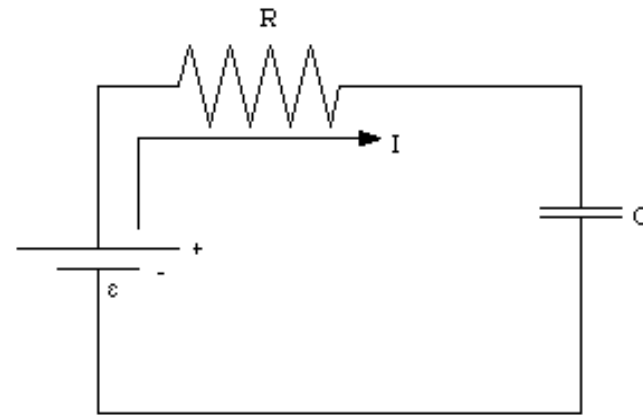- The rate at which capacitors charge and discharge can be calculated
- These curves are hyperbolic; they approach a limit (fully charged or fully discharged)




- The time constant of a circuit with capacitors and resistors (RC circuit) is:

$$T = R \cdot C$$

second

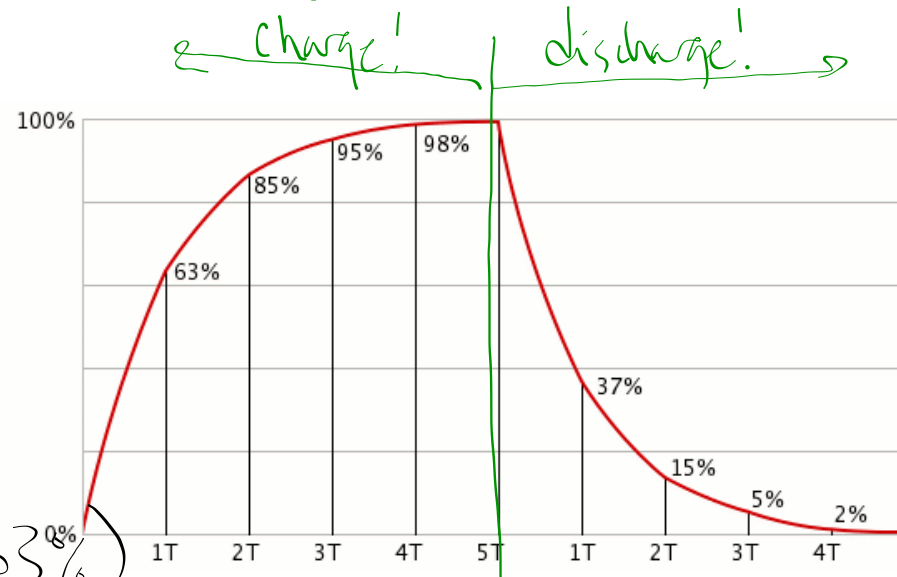(length of time to charge/discharge by 63%)




- It takes approximately 5 time constants to fully charge or fully discharge a capacitor

Cutoff Frequency:

- RC circuits can act as filters for AC voltages
- The cutoff frequency is the AC rate (in Hz) at which the signal starts to be decreased
- Many signals (like audio signals) consist of complex AC waveforms
- The formula for determining cutoff frequency is dependent on the time constant of the RC circuit:

$$f_{\text{cutoff}} = \frac{1}{2\pi R \cdot C}$$

Low pass filter

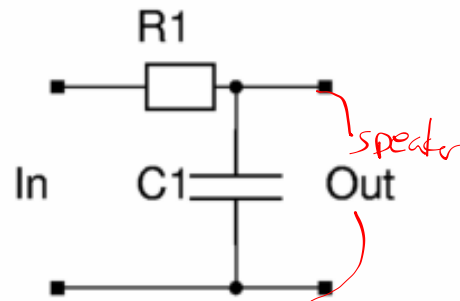

High pass filter

