

## Objectives:

- Students will understand equivalent resistance and how to calculate it
- Students will be able to analyze parallel circuits
- Students will be able to design simple parallel circuits

# Analyzing Parallel Circuits

- Start by finding "Equivalent Resistance" ( $R_{eq}$ )

- > For series paths, add the resistance together (do this first for all series paths!)
- > For parallel paths, there is a different formula:


$$\frac{1}{R_{tot}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots$$

$$R_{tot} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots}$$

- > If necessary, redraw the circuit to make  $R_{eq}$  clear
- > Continue finding  $R_{eq}$  for series and parallel paths as they emerge in your drawings

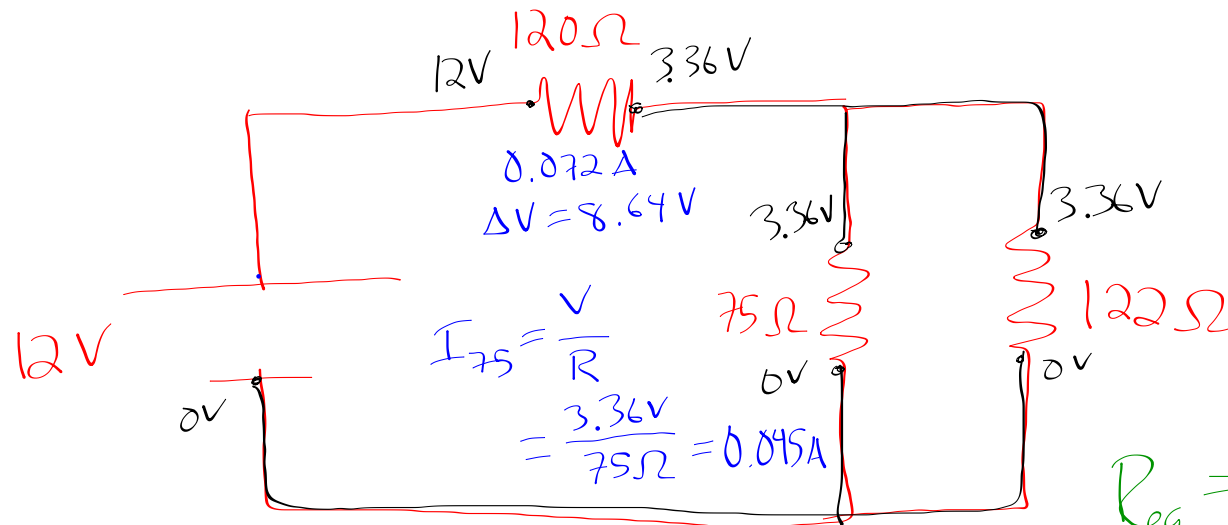
## Next ...

- After you've found  $R_{eq}$  for the entire circuit, you can find the total current ( $I_{tot}$ ) for the circuit
- Remember that current:
  - > Is always the same in series paths
  - > Is conserved at **junctions** (incoming current = outgoing current)
- Remember that voltage:
  - > Stays (roughly) the same in wires
  - > Drops through resistors and other components according to Ohm's Law
- Use Ohm's Law to find
  - > Voltage changes (usually the first step)
  - > Current through parallel paths
  - > Any other quantities




$$I_{122} = \frac{V}{R} = \frac{3.36V}{122\Omega} = 0.028A$$
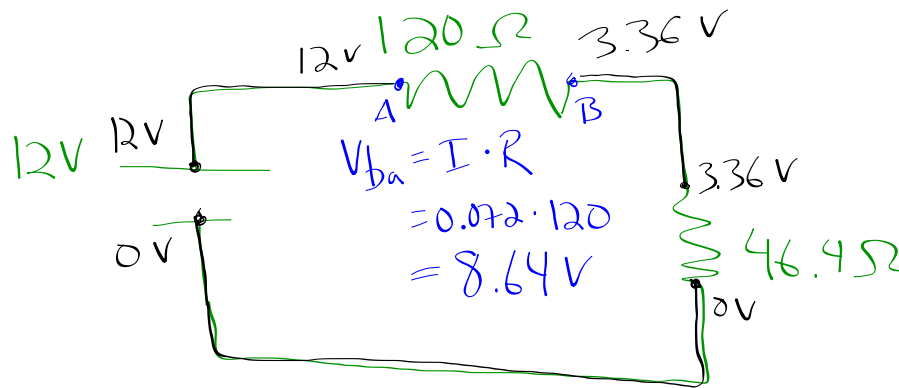
$$R_{eq} = \frac{1}{\frac{1}{75} + \frac{1}{122}} = 46.4\Omega$$




$$I = 0.072A$$

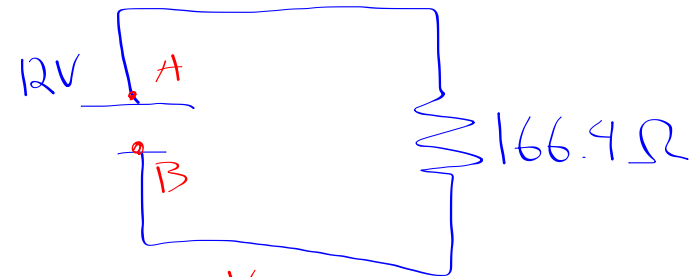

$$I_{tot} = \frac{V_{ba}}{R_{ba}} = \frac{12V}{166.4\Omega} = 0.072A$$

(72mA)

Example:

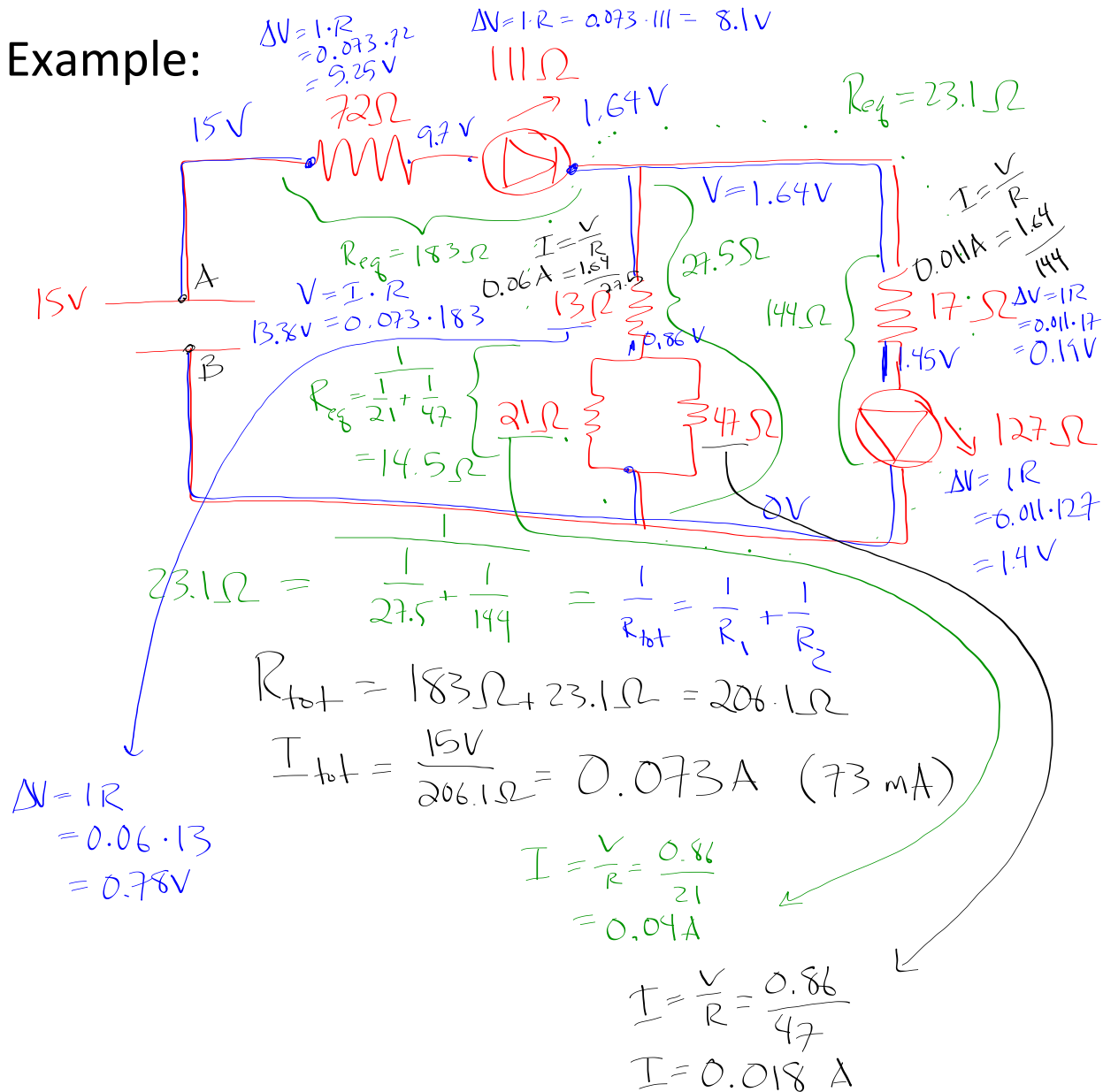

INDIVIDUALLY:

① Design & draw the circuit you proposed for the 1<sup>st</sup> part of the preliminary lab  
(5V, 15mA, 1 LED  $\cong$  200 $\Omega$ )

② Build & test (with LED) & measure

- draw  
if  $\rightarrow$  you want
- total current
- Voltage @ power supply (while on)
- calculate actual resistance of LED