

11/16/15 WHAT IS A BREADBOARD &
HOW IS IT USEFUL?

- TO MAKE A CIRCUIT, YOU NEED A CONDUCTING PATH THAT IS A COMPLETE LOOP.
- BREADBOARD ALLOW FOR EXPERIMENTATION OF CIRCUITS W/O THE NEED FOR SOLDERING OR LOTS OF ALLIGATOR CLIPS.
- FOR TEMPORARY CIRCUITS MADE WITH COMPONENTS THAT WILL BE RE-USED.

TODAY

- DRAW A DIAGRAM SHOWING HOW THE HOLES IN A BB ARE CONNECTED.
- SHOW DIAGRAM TO MR. K. OR MR. B.
- IF OKAY → YOU WILL MOVE ON