

5/16/16 OHM'S LAW REVIEW

$$V = IR$$

V = VOLTAGE (VOLTS) (V)

I = CURRENT (AMPS) (A)

R = RESISTANCE (OHMS) (Ω)

A 9 V BATTERY IS HOOKED TO THIS CIRCUIT. WHAT CURRENT RUNS THROUGH THE CIRCUIT?



~~~~~  
SOLUTION;

①  $V = 9V$   $R = 470\text{ k}\Omega$

$$470\text{ k}\Omega \left( \frac{1000\text{ }\Omega}{1\text{ k}\Omega} \right) = 470,000\text{ }\Omega$$

②  $I$

③  $V = IR$

④  $9 = I(470,000)$

⑤  $9 = \frac{I(470,000)}{470,000}$

$I = .00001915\text{ A}$

## TODAY

- ① FINISH YOUR DRAWING(S) FROM FRIDAY. THEY ARE DUE TODAY.  
(MUST BE APPROVED BEFORE TURNING IN)
- ② PICK A NEW PARTNER → SOMEONE YOU HAVE NOT WORKED WITH. → TELL MS. DALY.
- ③ GO TO SHOP & START.