

Analyzing Circuits with Capacitors (and Resistors...):


To analyze circuits with
RESISTORS, use:

$$V = I R$$

To analyze circuits with
CAPACITORS, use:

$$Q = C V$$

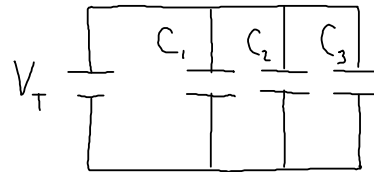Capacitors in Parallel -- finding the equivalent capacitance:



When hooked up to the battery, each capacitor acquires a charge.

In parallel, the voltage across each capacitor is the same:

$$V_T = V_1 = V_2 = V_3$$

The total charge that leaves the battery gets distributed to all capacitors:

$$Q_T = Q_1 + Q_2 + Q_3 \quad (\text{parallel})$$

$$\text{But } Q = CV$$

$$\therefore C_T V_T = C_1 V_1 + C_2 V_2 + C_3 V_3$$

$$C_T V_T = C_1 V_T + C_2 V_T + C_3 V_T$$


DIVIDING ALL TERMS BY V_T YIELDS:

$$C_T = C_1 + C_2 + C_3 + \dots$$

Capacitors in parallel are just added (think about the areas of the plates of each capacitor just merging)

The net effect of connecting capacitors in parallel is to increase the capacitance.

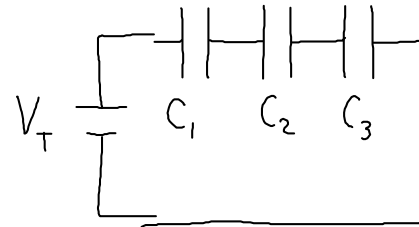Capacitors in Series -- finding the equivalent capacitance:



When hooked up to the battery, each capacitor acquires **the same** charge.

In series, the charge on each capacitor is the same:

$$Q_T = Q_1 = Q_2 = Q_3 \quad \text{in series}$$

The total voltage applied to the circuit must get distributed to all capacitors:

$$V_T = V_1 + V_2 + V_3$$

$$\text{But } Q = CV \quad \text{OR } V = Q/C$$

$$\therefore Q_T/C_T = Q_1/C_1 + Q_2/C_2 + Q_3/C_3$$

$$\frac{Q_T}{C_T} = \frac{Q_T}{C_1} + \frac{Q_T}{C_2} + \frac{Q_T}{C_3} \quad \text{DIVIDING ALL TERMS BY } Q_T$$

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$


For series:

$$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

The net effect of connecting capacitors in series is to decrease the capacitance.

EXAMPLE 1: What is the total charge delivered by the battery?

parallel

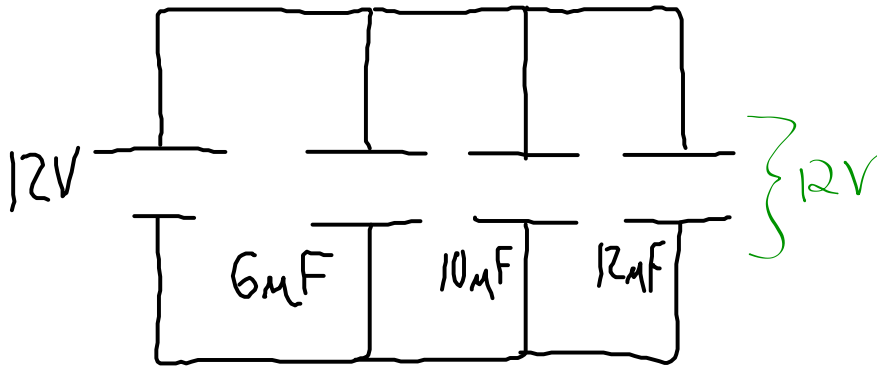


$$Q_T = Q_1 + Q_2 + Q_3$$

$$C_T = C_1 + C_2 + C_3$$

$$C_T = 28\mu\text{F}$$

$$Q = CV = (28 \times 10^{-6})(12) \\ = \boxed{3.36 \times 10^{-4} \text{ C}}$$

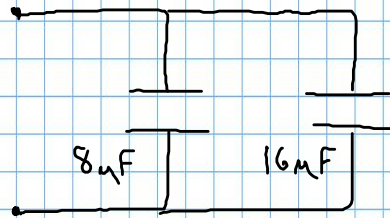EXAMPLE 2: What is the charge on the $8\mu\text{F}$ capacitor?




$$Q_{16} = 10\mu\text{C}$$

$$V_T = V_8 = V_{16} = \frac{Q_{16}}{C_{16}} = \frac{10\mu\text{C}}{16\mu\text{F}} = .625\text{V}$$

$$Q_8 = C_8 V_8 = (8 \times 10^{-6}) (.625) = \boxed{5.0 \times 10^{-6} \text{ C}}$$

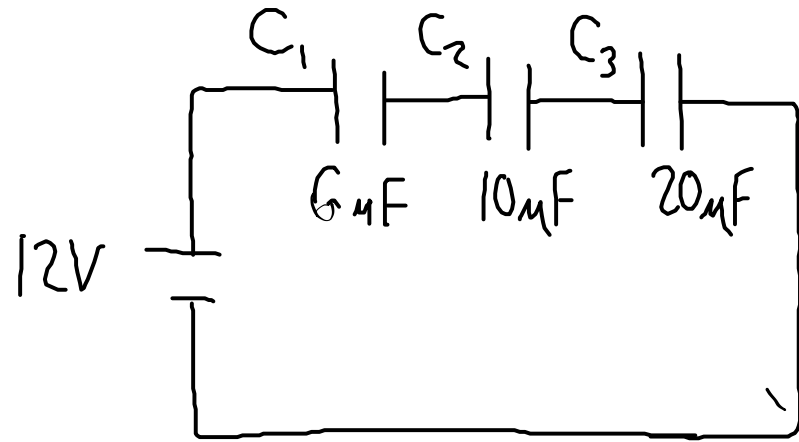EXAMPLE 3: What is the charge delivered by the battery?



series

$$V_T = V_1 + V_2 + V_3$$

$$Q_1 = Q_2 = Q_3$$

$$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

$$C_T = 3.16e^{-6} \text{ F}$$


$$3.8e^{-6} \text{ C}$$

$$Q = CV$$

$$= (3.16e^{-6})12$$

$$Q_T = 3.79e^{-5} \text{ C}$$

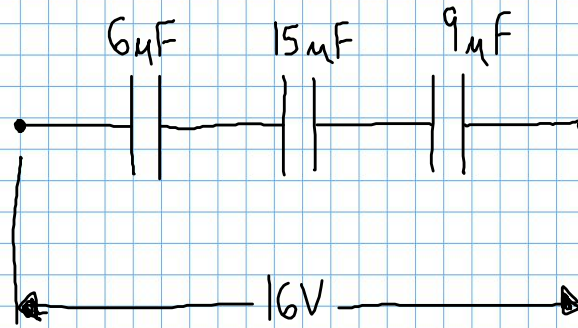EXAMPLE 4: What is the potential difference across the 15 μ F capacitor?



$$V_{15} = Q_{15} / C_{15}$$

FIND Q_{15} :


$$\frac{1}{C_T} = \frac{1}{6\mu F} + \frac{1}{15\mu F} + \frac{1}{9\mu F}$$

$$C_T = 2.90\mu F$$


$$\begin{aligned} Q_6 = Q_{15} = Q_9 = Q_T &= C_T V_T \\ &= (2.9 \times 10^{-6})(16) \\ &= 4.65 \times 10^{-5} C \end{aligned}$$

$$V_{15} = \frac{Q_{15}}{C_{15}} = \frac{4.65 \times 10^{-5}}{15 \times 10^{-6}} = \boxed{3.10 V}$$

EXAMPLE 5: What is the equivalent total capacitance of this circuit?

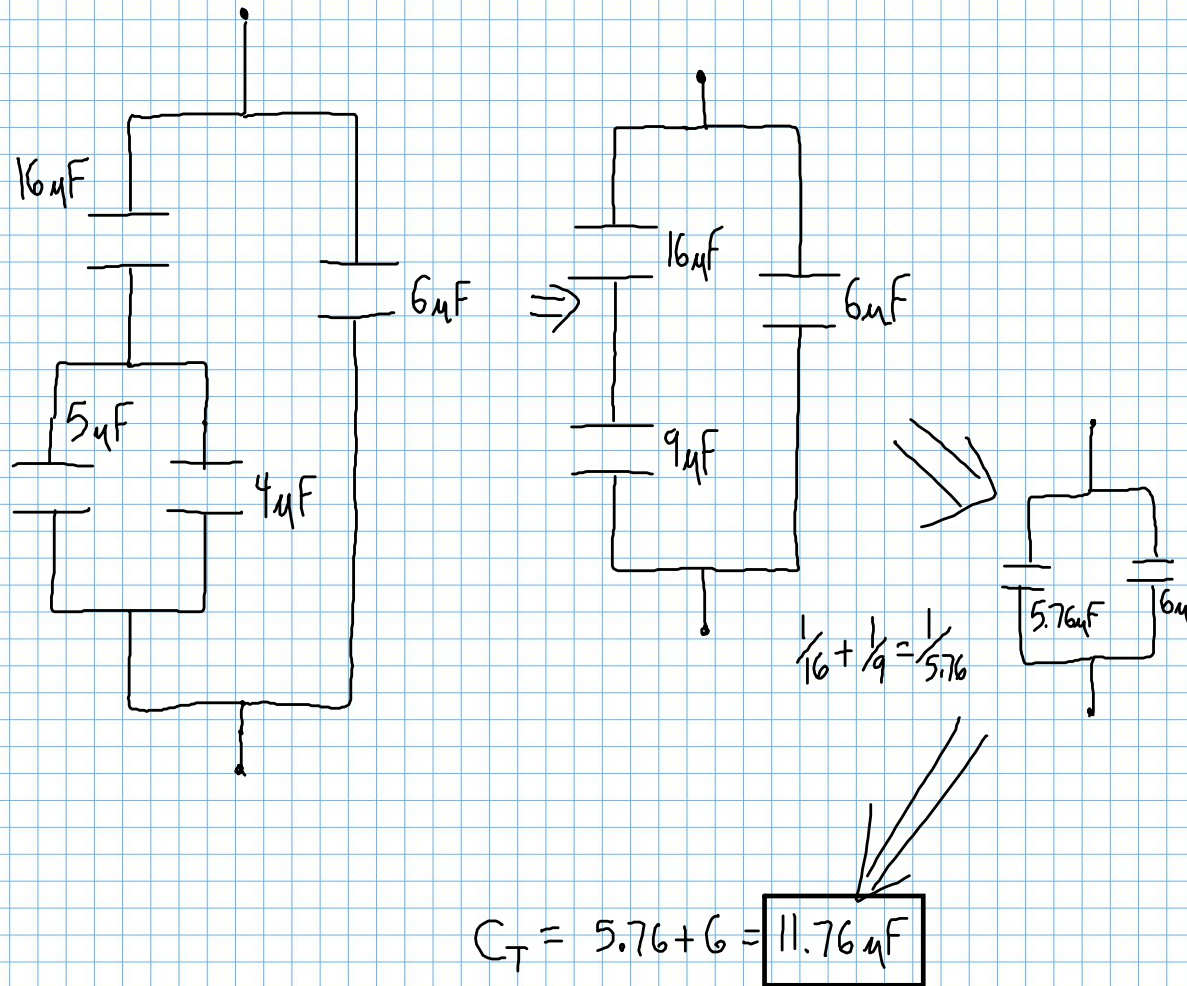

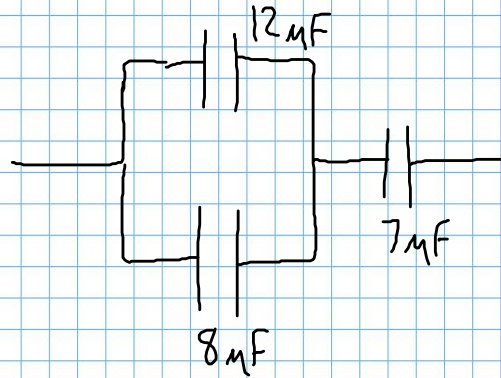EXAMPLE 6: Find Q_{12} and V_7 given that $Q_8 = 5 \mu\text{C}$.



$$\frac{Q_8}{C_8} = V_8 = \frac{5 \times 10^{-6}}{8 \times 10^{-6}} = .625 \text{ V}$$



$$V_{12} = V_8 = .625 \text{ V}$$

$$Q_{12} = C_{12} V_{12} = (12 \times 10^{-6}) (.625) = 7.5 \times 10^{-6} \text{ C} = \boxed{7.5 \mu\text{C}}$$

$$Q_7 = Q_T = Q_8 + Q_{12} = 5 \mu\text{C} + 7.5 \mu\text{C} = 12.5 \mu\text{C}$$

$$V_7 = \frac{Q_7}{C_7} = \frac{12.5 \mu\text{C}}{7 \mu\text{F}} = \boxed{1.79 \text{ V}}$$

Resistors and Capacitors TOGETHER

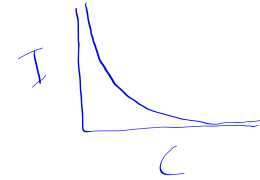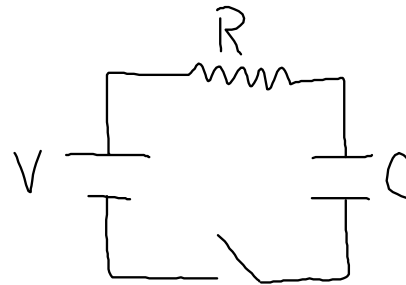

When the switch is initially closed, there is no charge on C .

As a result, effectively C has no resistance to current flow.

As C charges, the current decreases until it drops to zero when the capacitor has become fully charged.

The thing to understand about capacitors with resistors in DC circuits:

Initially, immediately after the circuit is turned on:

1. C has no charge
2. C has no resistance
3. Treat the circuit like C does not exist.


After the capacitor has become fully charged:

1. C has a voltage
2. C has infinite resistance
3. No current flows through C or anything in series with C

} "STEADY STATE"

→ No current through any path that has a capacitor

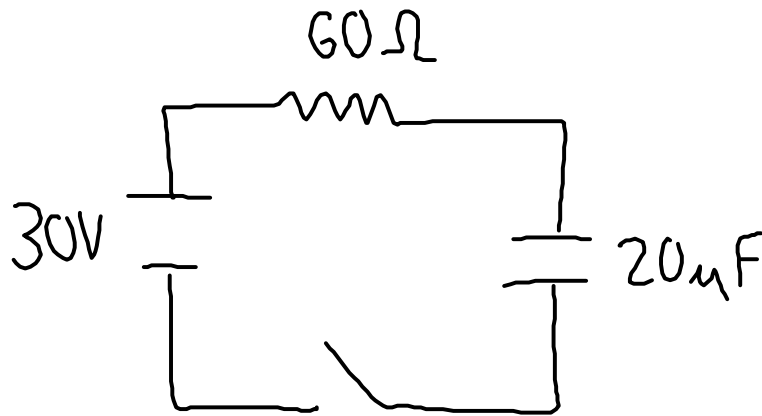EXAMPLE 7: What is the current through the resistor before the capacitor has any charge, and after the capacitor has become fully charged?



Start: $R_C = 0$

$$V = IR$$
$$30 = I(60)$$
$$I = 0.5A$$



End: $R_C = \infty$

$$I = 0A$$

EXAMPLE 8: Find I in the 12 Ohm resistor

a) Initially

b) After a long time

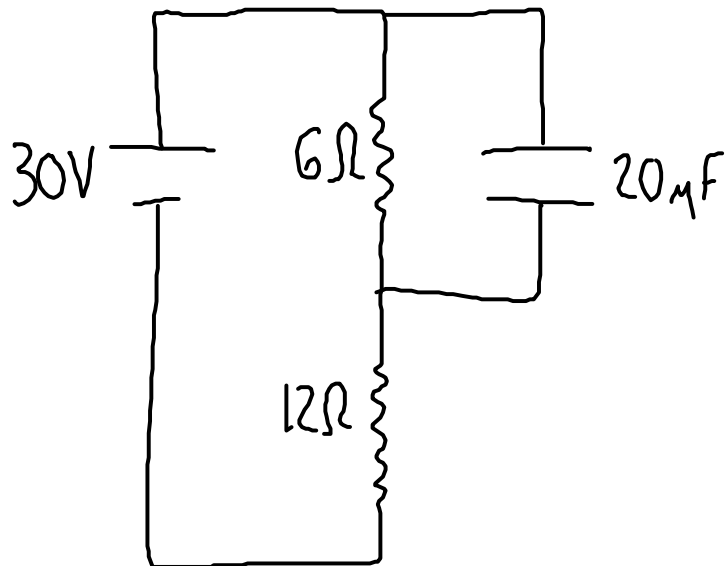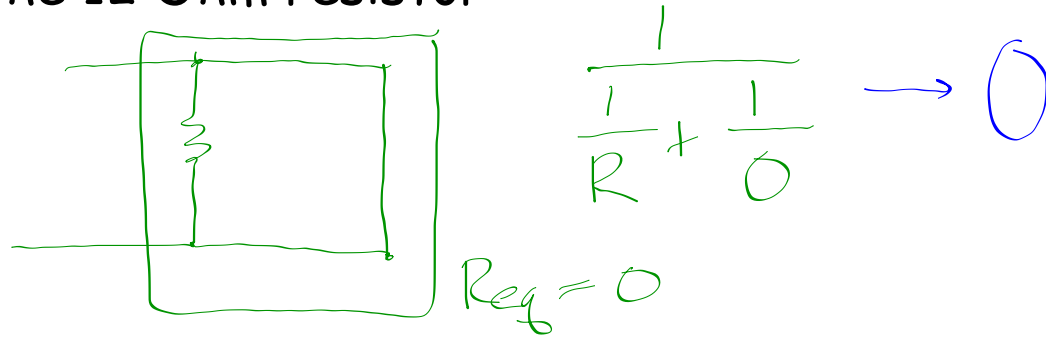

a) $V = IR$
 $30 = I(12)$
 $I = 2.5 \text{ A}$

b) $V = IR$
 $30 = I(18)$
 $I = 1.67 \text{ A}$