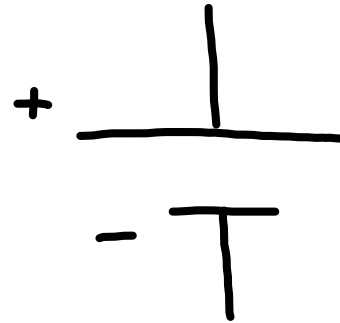


# 11/29/17 SCHEMATIC DIAGRAMS

- ITS A SIMPLIFIED PICTURE OF A CIRCUIT.
- IT SHOWS THE LOGIC IN A CIRCUIT.  
(THE ORDER THAT COMPONENTS ARE CONNECTED, ETC...)
- IT DOES NOT SHOW HOW THE CIRCUIT PHYSICALLY LOOKS.


BATTERY






RESISTOR



LIGHT BULB  
(INCANDESCENT)

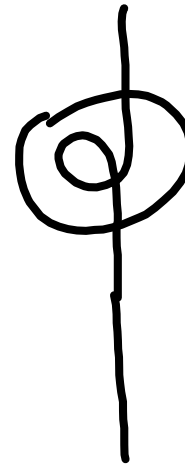

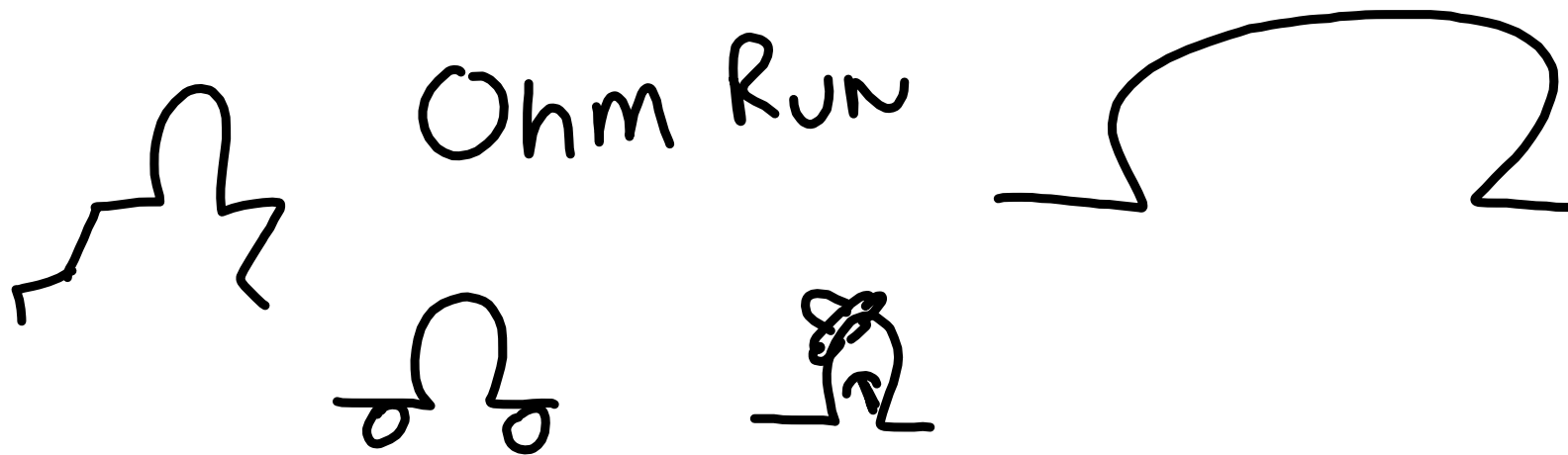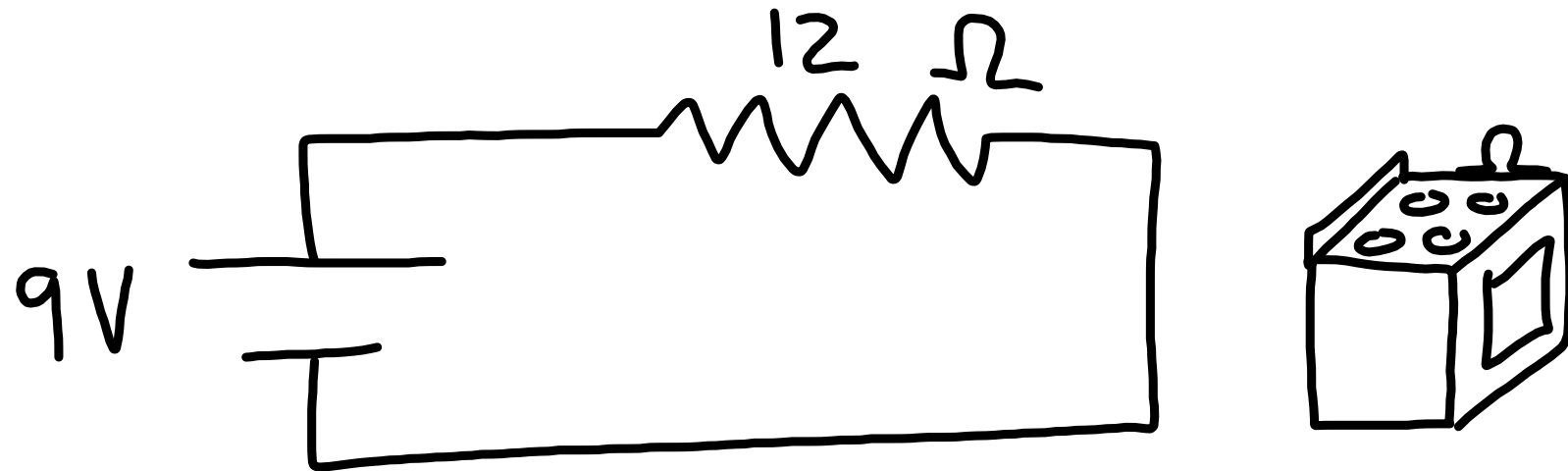

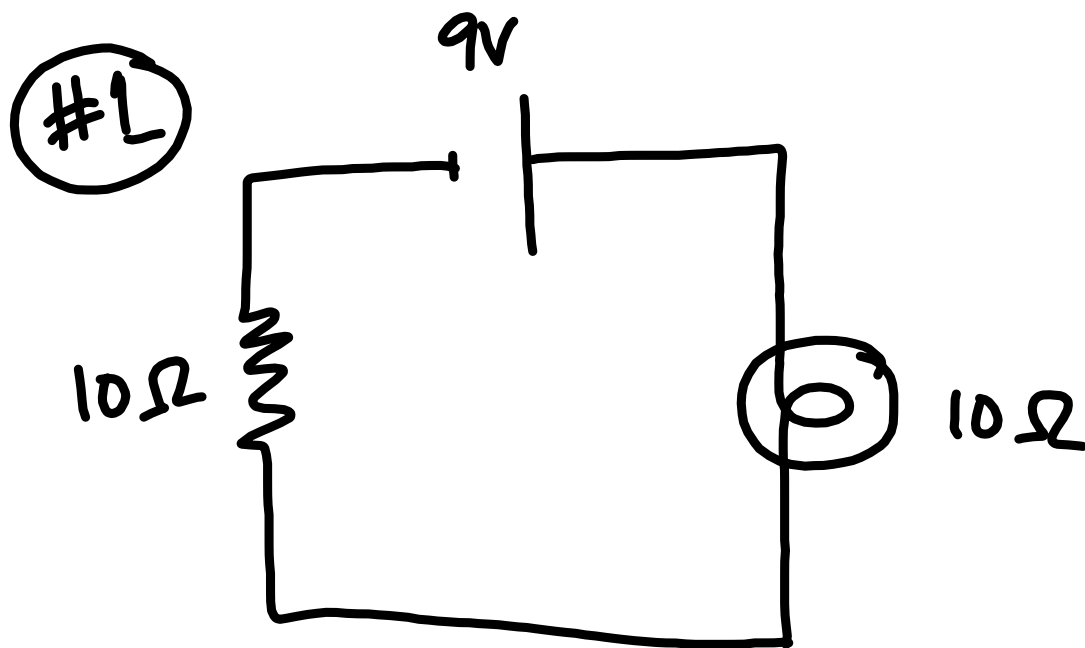

Dan Bregar  
Virtual circuits