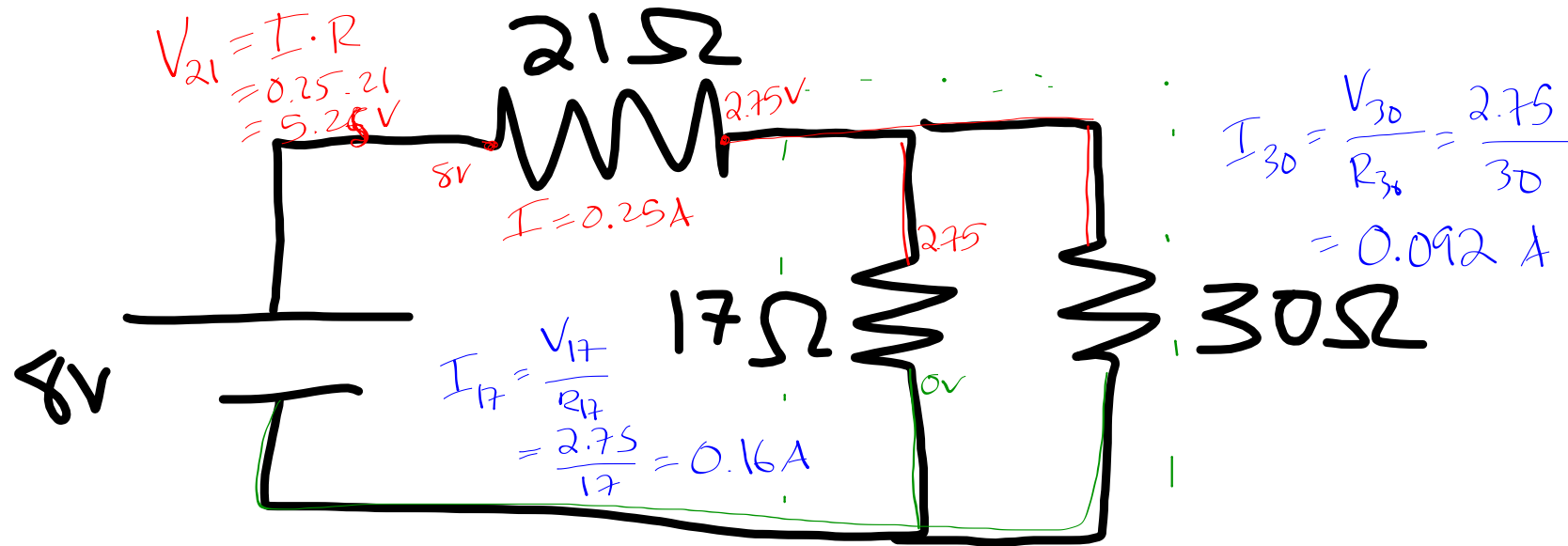


START FRIDAYrun into Tuesday?


- SOLVE CIRCUITS \rightarrow find I , V through each component & path given power supply voltage & resistance
- Use the meter to measure R , I , V of real circuits & components



$$R_{TOT} = 21\Omega + 10.9\Omega = 31.9\Omega$$

$$R_{eq} = \frac{1}{\frac{1}{17} + \frac{1}{30}} = 10.9\Omega$$
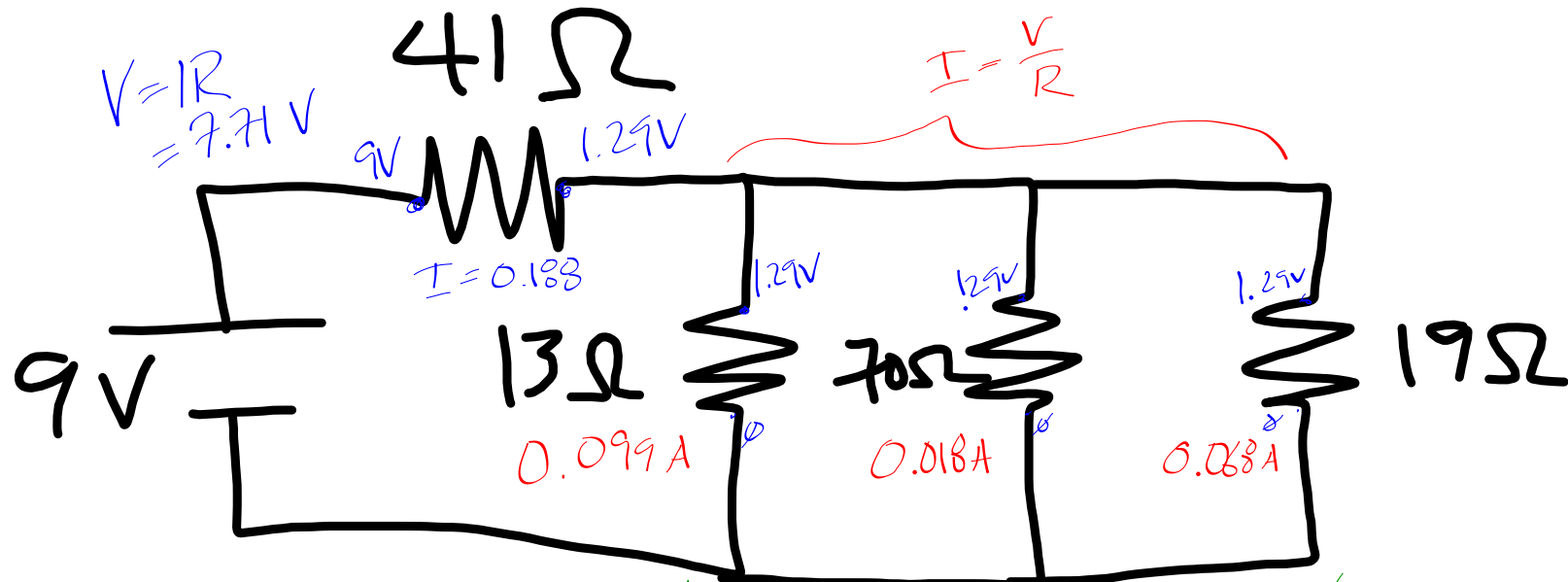
$$I_{TOT} = \frac{V_{TOT}}{R_{TOT}} = \frac{8\text{V}}{31.9\Omega} = 0.25\text{A}$$



$$R_{TOT} = 41 + 6.95 = 47.95 \Omega$$

$$I_{TOT} = \frac{V}{R} = 0.188 A$$

$$R_{eq} = \frac{1}{\frac{1}{13} + \frac{1}{70} + \frac{1}{19}} = 6.95 \Omega$$

