

OHM'S LAW


$$V = I \cdot R$$

Volts, $\frac{J}{C}$ \downarrow \rightarrow Ohms, Ω

Current \rightarrow Amperes (amps)
C/s

$$V_{ba} = I_{a \rightarrow b} \cdot R_{a \rightarrow b}$$

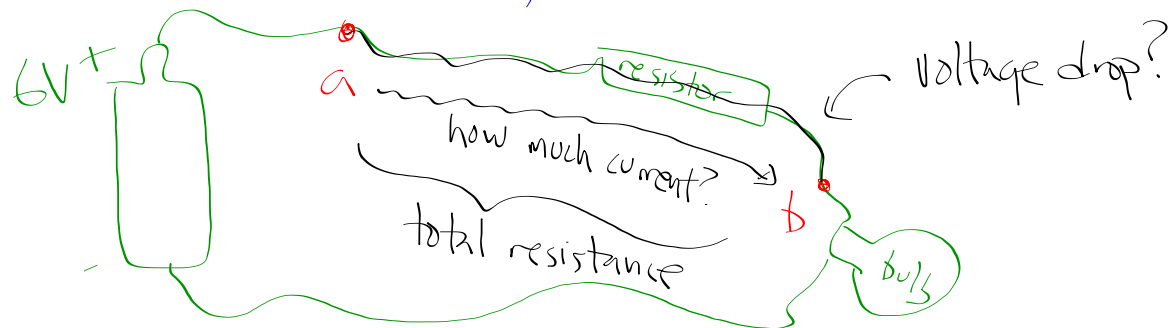(voltage change) (current through a section) (total resistance)



Measuring voltage

set dial to
AC (power
socket)

DC (everything
else)

set high
1st & adjust
downwards

⊕ POLARITY

+ 0 red lead (positive)

- 0 black lead (negative)

Put red lead at
higher voltages &
black lead at
lower voltages.

Meter will tell you

V_{ba}

Measuring Resistance

set to

Ω -

$\times 10k$

1st ξ adjust

downwards

\oplus POLARITY

$+$

$-$

red lead (positive)

black lead (negative)

You have to
measure resistance
of a disconnected
component/path.

- NO LIVE CIRCUITS
- ONLY ONE PATH

Measuring current

Start dial
at "0.3 A"
and reduce
as needed

⊕

polarity

⊕

red lead

⊖

black lead

The meter will be
part of your circuit!

You'll break your
circuit, then use
the meter like wire.

(Red goes closest to
⊕, black goes closest
to ⊖)

